

29. (a) $I_1 = \frac{V}{R_1} = \frac{20 \text{ V}}{20 \Omega} = \boxed{1.0 \text{ A}}$. R_2 and R_3 are in series: $R_s = 20 \Omega + 20 \Omega = 40 \Omega$.

So $I_2 = I_3 = \frac{20 \text{ V}}{40 \Omega} = \boxed{0.50 \text{ A}}$.

(b) $V_1 = \boxed{20 \text{ V}}$, $V_2 = V_3 = I_2 R_2 = (0.50 \text{ A})(20 \Omega) = \boxed{10 \text{ V}}$.

(c) The total power is $P = \frac{V^2}{R_1} + \frac{V^2}{R_s} = \frac{(20 \text{ V})^2}{20 \Omega} + \frac{(20 \text{ V})^2}{40 \Omega} = \boxed{30 \text{ W}}$.

37. (a) R_1 and R_2 are in series. $R_{s1} = 10 \Omega + 5.0 \Omega = 15 \Omega$.

So $I_1 = I_2 = \frac{V}{R_{s1}} = \frac{10 \text{ V}}{15 \Omega} = \boxed{0.67 \text{ A}}$ $I_3 = \frac{10 \text{ V}}{10 \Omega} = \boxed{1.0 \text{ A}}$.

R_4 and R_5 are in series. $R_{s2} = 5.0 \Omega + 20 \Omega = 25 \Omega$. So $I_4 = I_5 = \frac{10 \text{ V}}{25 \Omega} = \boxed{0.40 \text{ A}}$.

(b) $V_1 = I_1 R_1 = (0.667 \text{ A})(10 \Omega) = \boxed{6.7 \text{ V}}$, $V_2 = (0.667 \text{ A})(5.0 \Omega) = \boxed{3.3 \text{ V}}$, $V_3 = \boxed{10 \text{ V}}$,

$V_4 = (0.40 \text{ A})(5.0 \Omega) = \boxed{2.0 \text{ V}}$, $V_5 = (0.40 \text{ A})(20 \Omega) = \boxed{8.0 \text{ V}}$.

97. (a) R_2 , R_3 , and R_4 are in parallel combination,

$$\frac{1}{R_p} = \frac{1}{25 \Omega} + \frac{1}{50 \Omega} + \frac{1}{25 \Omega} = \frac{1}{10 \Omega}, \quad \text{so } R_p = 10 \Omega.$$

So the total current is $I = I_1 = \frac{110 \text{ V}}{100 \Omega + 10 \Omega} = \boxed{1.0 \text{ A}}$.

The voltage on R_p is $(1.0 \text{ A})(10 \Omega) = 10 \text{ V}$.

Therefore $I_2 = I_4 = \frac{10 \text{ V}}{25 \Omega} = \boxed{0.40 \text{ A}}$, $I_3 = \frac{10 \text{ V}}{50 \Omega} = \boxed{0.20 \text{ A}}$.

(b) $P_1 = I^2 R_1 = (1.0 \text{ A})^2 (100 \Omega) = \boxed{100 \text{ W}}$, $P_2 = P_4 = (0.40 \text{ A})^2 (25 \Omega) = \boxed{4.0 \text{ W}}$,

$P_3 = (0.20 \text{ A})^2 (50 \Omega) = \boxed{2.0 \text{ W}}$.

99. Use the results in Exercise 18.98,

The current through the first two R 's (from left) is

$$I_1 = I_2 = \frac{V}{R_{s3}} = \frac{12.0 \text{ V}}{2.73(10.0 \Omega)} = \boxed{0.440 \text{ A}}.$$

The voltage across R_{p2} is $V_{p2} = I_1 R_{p2} = (0.440 \text{ A}) \frac{11}{15} (10.0 \Omega) = 3.23 \text{ V}$.

So the current through the third R is $I_3 = \frac{3.23 \text{ V}}{10.0 \Omega} = \boxed{0.323 \text{ A}}$.

The current through the next two R 's is $I_4 = I_5 = \frac{3.23 \text{ V}}{11(10.0 \Omega)/4} = \boxed{0.117 \text{ A}}$.

The voltage across R_{p1} is $V_{p1} = I_4 R_{p1} = (0.117 \text{ A}) \frac{3}{4} (10.0 \Omega) = 0.878 \text{ V}$.

So $I_6 = \frac{0.878 \text{ V}}{10.0 \Omega} = \boxed{0.0878 \text{ A}}$, $I_7 = I_8 = I_9 = \frac{0.878 \text{ V}}{3(10.0 \Omega)} = \boxed{0.0293 \text{ A}}$.

61. $P = \frac{V^2}{R}$, $\Rightarrow R = \frac{V^2}{P} = \frac{(120 \text{ V})^2}{100 \text{ W}} = \boxed{144 \Omega}$.

62. $P = \frac{V^2}{R} = \frac{(110 \text{ V})^2}{10 \Omega} = \boxed{1.2 \times 10^3 \text{ W}}$.

63. $P = I^2 R = (13 \text{ A})^2 (12 \Omega) = \boxed{2.0 \times 10^3 \text{ W}}$.

65. $P = \frac{V^2}{R}$, $\Rightarrow R = \frac{V^2}{P} = \frac{(240 \text{ V})^2}{50 \times 10^3 \text{ W}} = \boxed{1.2 \Omega}$.

68. (a) $I = \frac{V}{R} = \frac{1.50 \text{ V}}{2.50 \Omega} = \boxed{0.600 \text{ A}}$.

(b) $q = It = (0.600 \text{ A})(6.00 \text{ h})(3600 \text{ s/h}) = \boxed{1.30 \times 10^4 \text{ C}}$.

(c) $E = qV = (1.30 \times 10^4 \text{ C})(1.50 \text{ V}) = \boxed{1.94 \times 10^4 \text{ J}}$.

Alternate method: $E = pt = I^2 R t = (0.600 \text{ A})^2 (2.50 \Omega)(6.00 \text{ h})(3600 \text{ s/h}) = 1.94 \times 10^4 \text{ J}$.

69. (a) $E = Pt = IVt = (18 \text{ A})(240 \text{ V})(1.0 \text{ s}) = \boxed{4.3 \times 10^3 \text{ J}}$.

(b) $R = \frac{V}{I} = \frac{240 \text{ V}}{18 \text{ A}} = \boxed{13 \Omega}$.

70. (a) $E = P t = (4.5 \text{ kW})(2.0 \text{ h/d})(30 \text{ d}) = 270 \text{ kWh}$.

So it costs $(270 \text{ kWh})(15 \text{ ¢/kWh}) = \boxed{\$40.50}$.

(b) From Table 17.2, a water heater draws 37.5 A at 240 V. So $R = \frac{V}{I} = \frac{240 \text{ V}}{37.5 \text{ A}} = \boxed{6.4 \Omega}$.

82. (a) The input power to the pump is $P = \frac{2.00 \text{ kW}}{0.84} = 2.38 \text{ kW}$.

$P = VI$, $\Rightarrow I = \frac{P}{V} = \frac{2.38 \times 10^3 \text{ W}}{240 \text{ V}} = \boxed{9.9 \text{ A}}$.

(b) $R = \frac{V}{I} = \frac{240 \text{ V}}{9.9 \text{ A}} = \boxed{24 \Omega}$.

35. (a) The wattage ratings are based on 120 V. $P = \frac{V^2}{R}$, $\Rightarrow R = \frac{V^2}{P}$.

$R_{15} = \frac{(120 \text{ V})^2}{15 \text{ W}} = 960 \Omega$, $R_{40} = \frac{(120 \text{ V})^2}{40 \text{ W}} = 360 \Omega$, $R_{60} = \frac{(120 \text{ V})^2}{60 \text{ W}} = 240 \Omega$,

and $R_{100} = \frac{(120 \text{ V})^2}{100 \text{ W}} = 144 \Omega$. So the equivalent resistance is

$R_{\text{eq}} = 960 \Omega + 360 \Omega + \frac{(240 \Omega)(144 \Omega)}{240 \Omega + 144 \Omega} = 1410 \Omega$. Therefore $I = \frac{V}{R_{\text{eq}}} = \frac{120 \text{ V}}{1410 \Omega} = \boxed{0.085 \text{ A}}$.

(b) $P_{15} = I^2 R = (0.0851 \text{ A})^2 (960 \Omega) = \boxed{7.0 \text{ W}}$, $P_{40} = (0.851 \text{ A})^2 (360 \Omega) = \boxed{2.6 \text{ W}}$.

$$V_{60} = V_{100} = 120 \text{ V} - (0.0851 \text{ A})(960 \Omega + 360 \Omega) = 7.67 \text{ V}.$$

$$\text{So } P_{60} = \frac{V^2}{R} = \frac{(7.67 \text{ V})^2}{240 \Omega} = \boxed{0.24 \text{ W}}, \quad P_{100} = \frac{(7.67 \text{ V})^2}{144 \Omega} = \boxed{0.41 \text{ W}}.$$